



Electronic Engineering Club

First Semester Post-Mortem and Second Semester Look-Ahead

Outline

- **First Semester:**
Foundations of Analog Electronics
- **Second Semester:**
Entering the Digital World

Electronic Engineering Club

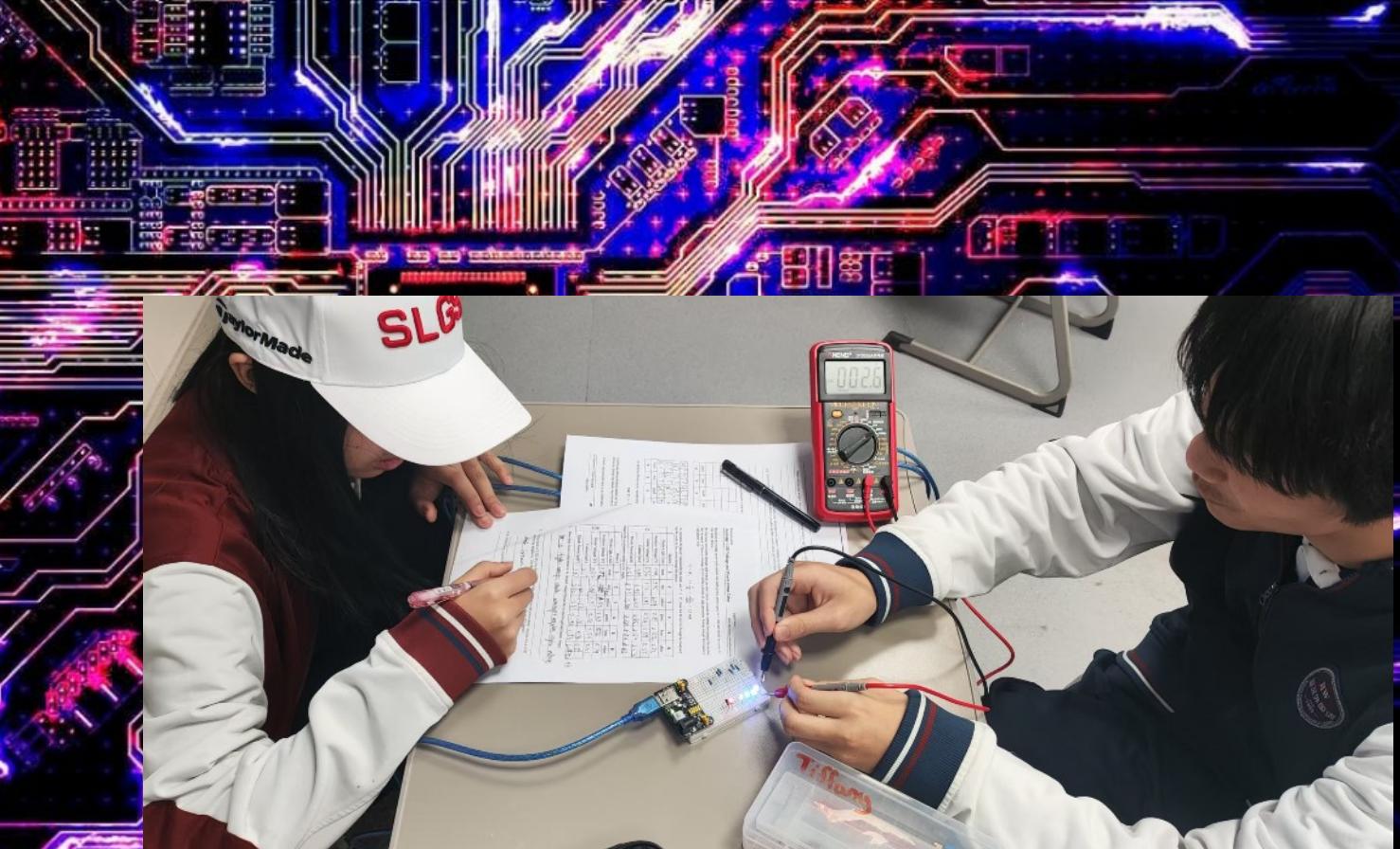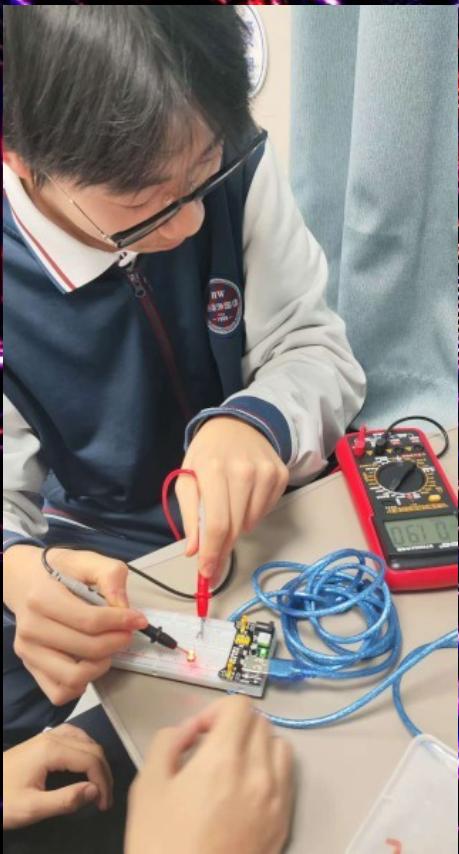

Foundations of Analog Electronics

- Resistors
- Current and Voltage
- Capacitors
- Diodes
- Transistors

Understanding Capacitance


- A **resistor** is an electronic component that inhibits the flow of electricity
 - it acts like a valve controlling the amount of current flow



resistor

Understanding Resistance

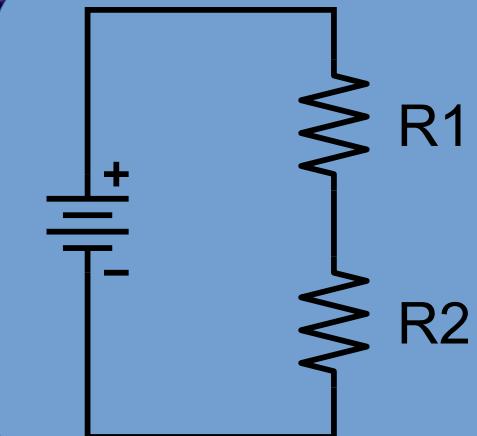
- Learning objective completed:
 - Understand and calculate the **total resistance** of resistors in a **series circuit**.




$$R_T = \sum_n R_n$$

Understanding Resistance

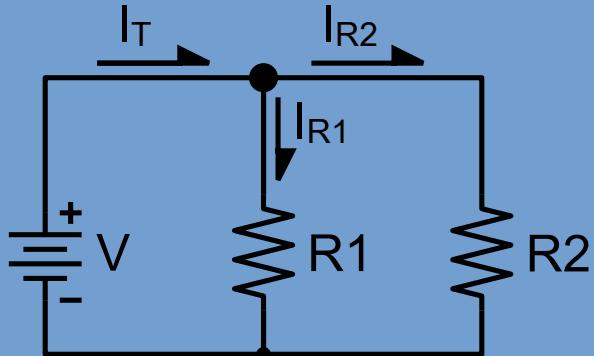- Learning objective completed:
 - Understand and calculate the **total resistance** of resistors in a **parallel circuit**.





$$\frac{1}{R_T} = \sum_n \frac{1}{R_n}$$

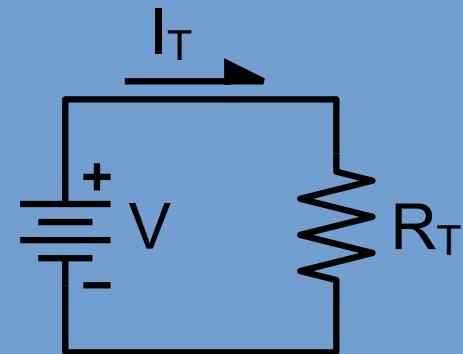

Understanding Resistance

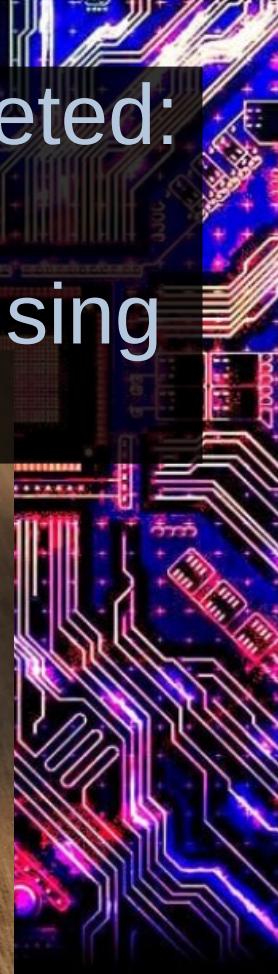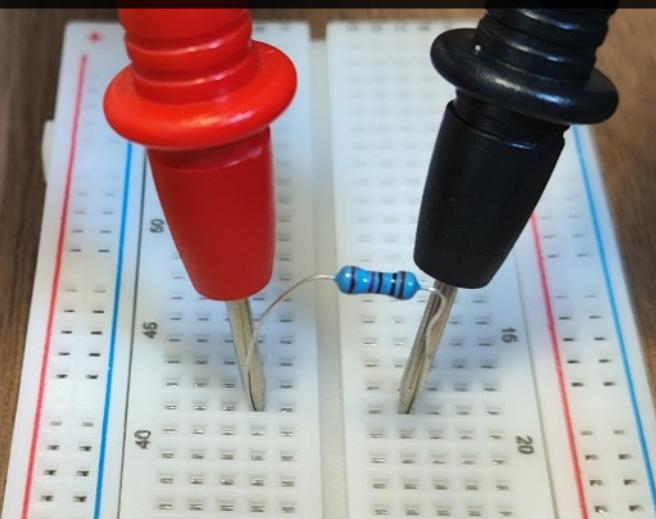- Learning objective completed:
 - Safely and accurately **measure resistance** using a multimeter



Understanding Voltage and Current

- **Current** is the number of electrons flowing through a circuit per unit time.
-
- **Voltage** is the pressure that pushes these electrons

$$I = \frac{Q}{t}$$



Analogy:

- Water flowing through the hose represents the **current**.
- The pressure pushing the water represents the **voltage**.



Ohm's Law

- Learning objective completed:
 - Understand **Ohm's Law**, $V = I \cdot R$, the relationship between voltage, resistance and electrical current
 - Use ohms law to **calculate voltage, current, and resistance** values in electronic circuits





Understanding Voltage

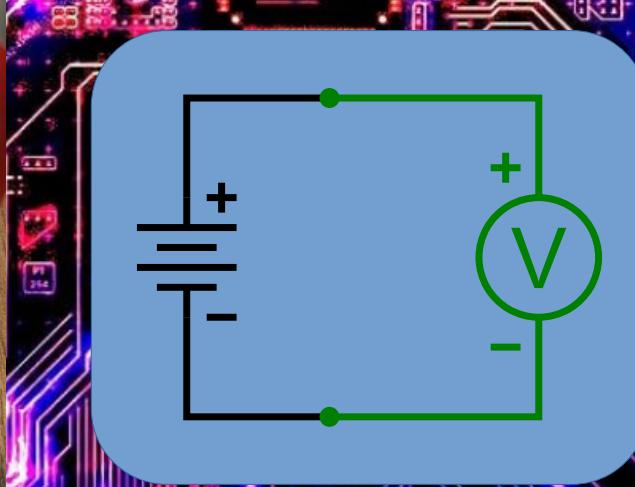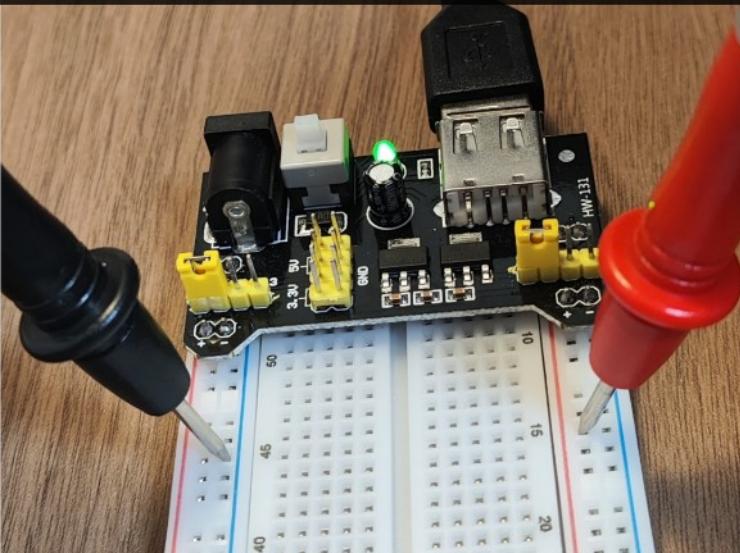- Learning objective completed:
 - Safely measure voltage using a multimeter




Understanding Voltage

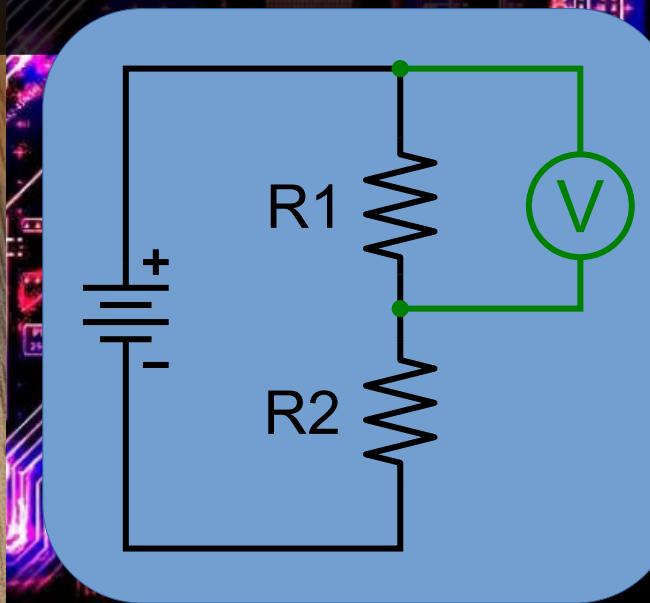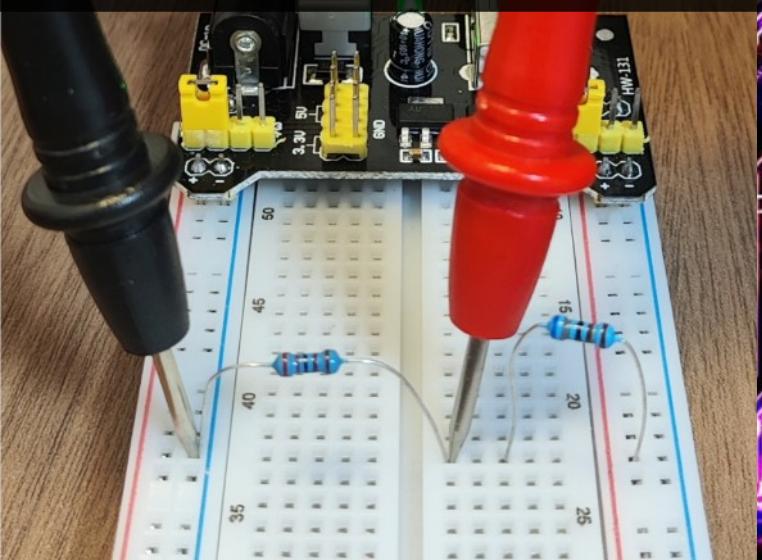- Learning objective completed:
 - Safely measure **voltage** across **components** of a circuit






Understanding Capacitance

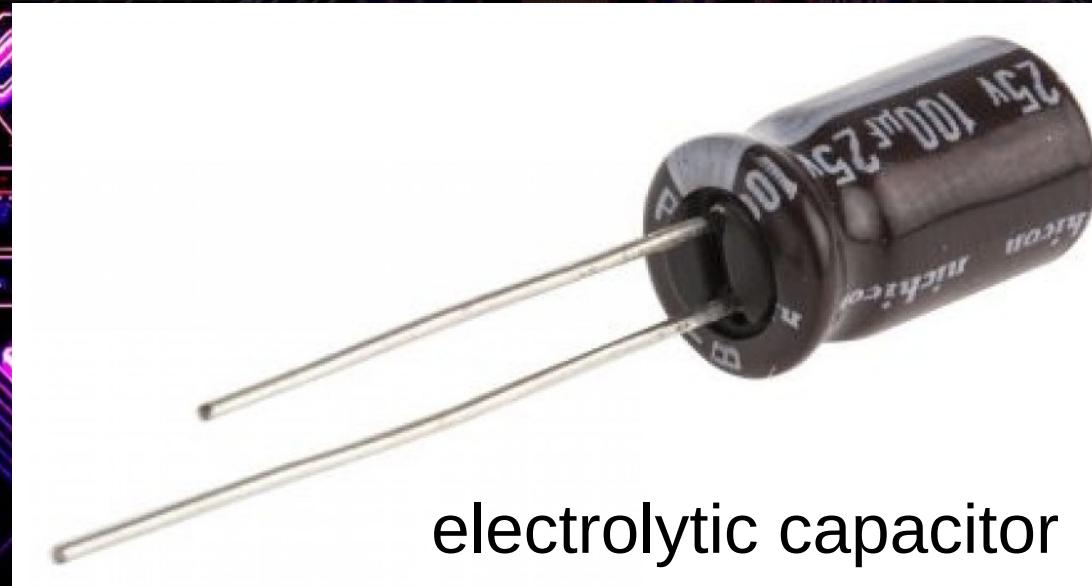- A **capacitor** is an electronic component that stores electrical charge
 - It acts like a small, fast battery




Understanding Capacitance

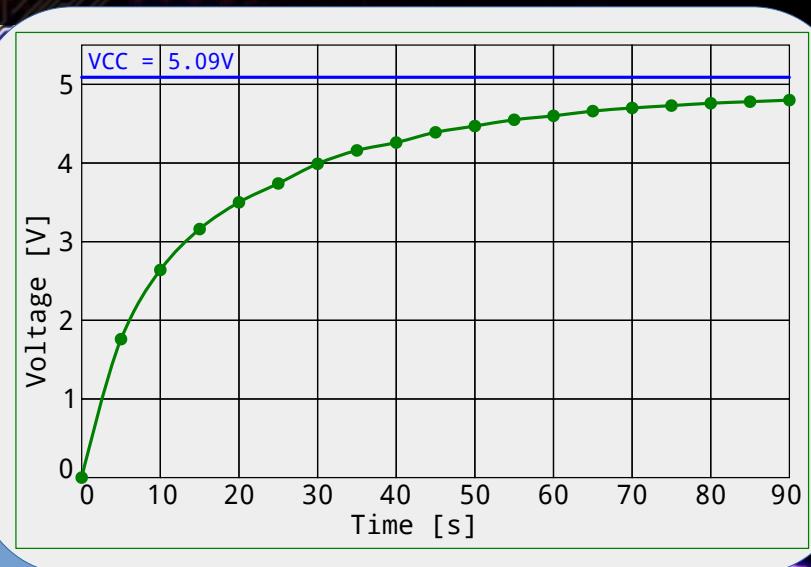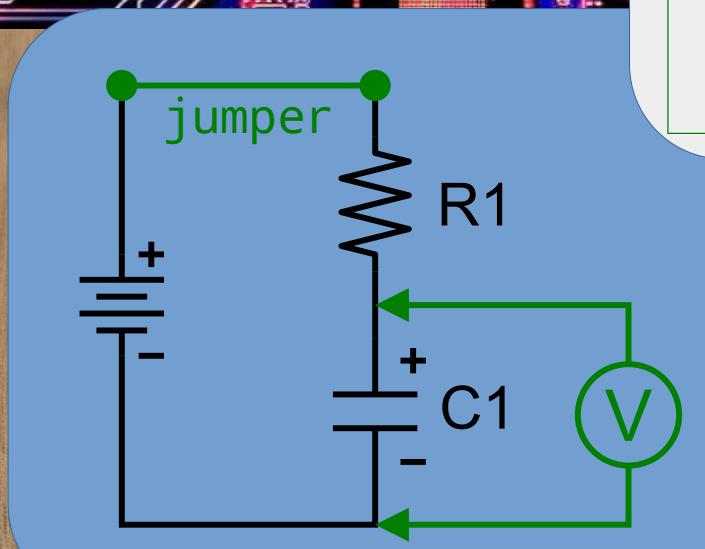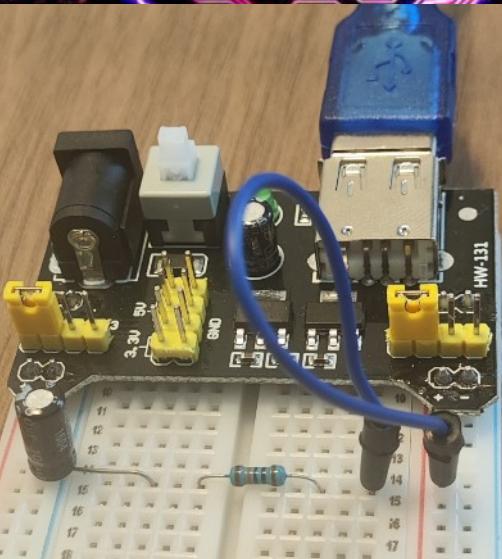- Learning objective completed:
 - Safely measure **change in voltage** across a **charging capacitor** in an RC circuit




Understanding Capacitance

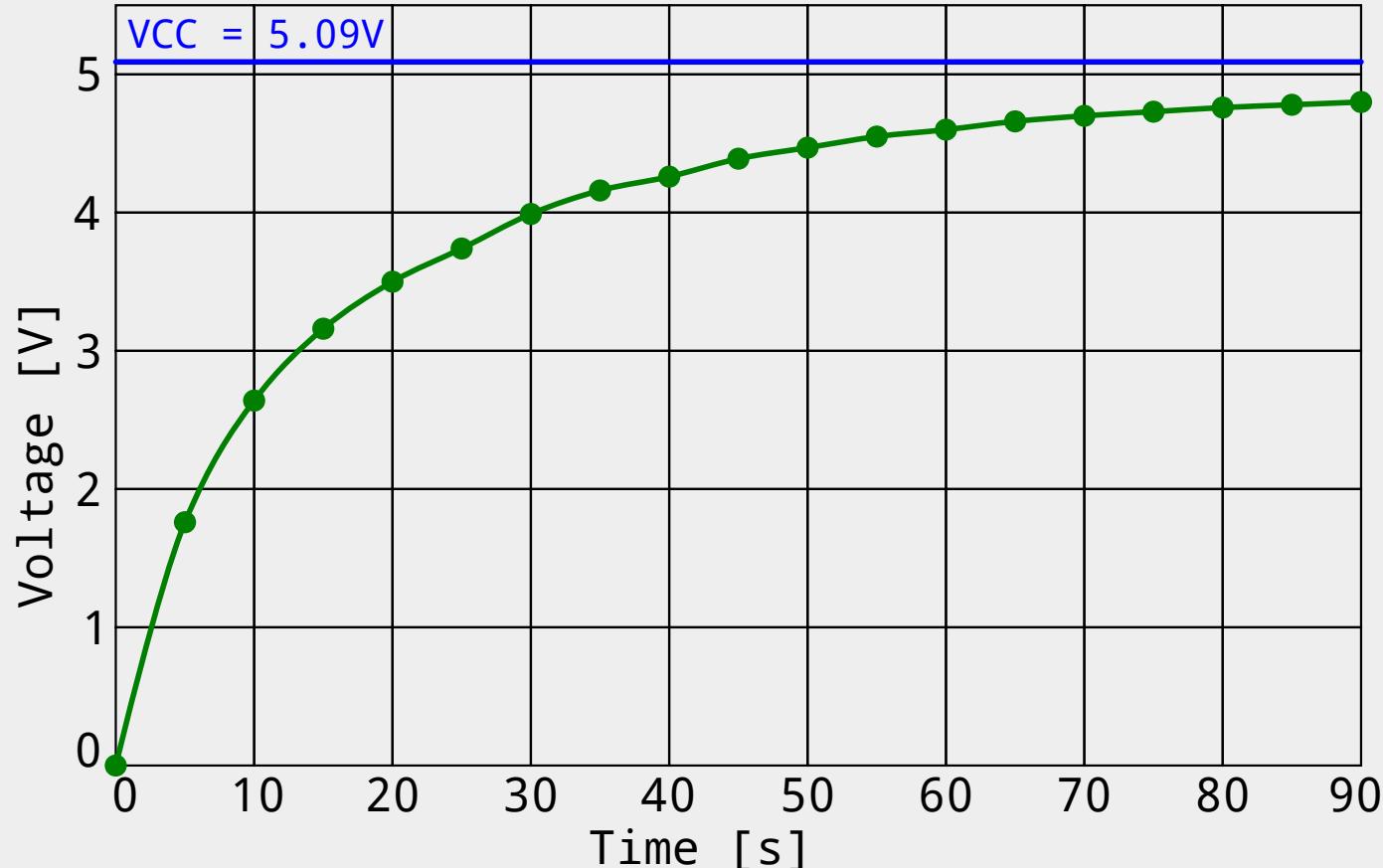



Understanding Diodes

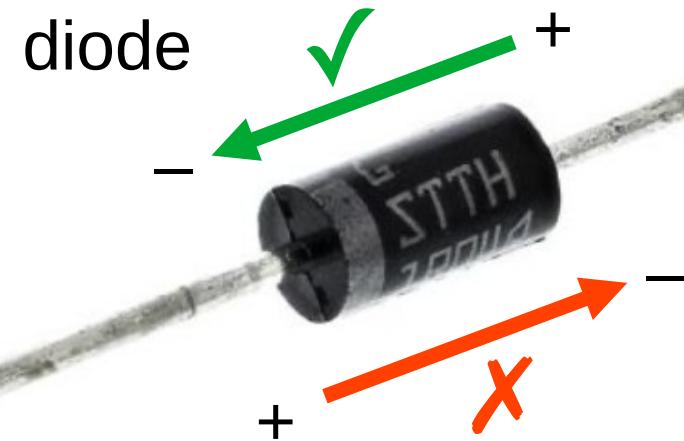- A **diode** is a semiconductor that allows current to flow in only one direction
 - Diodes are used in circuits that convert AC to DC (such as USB chargers).




Understanding Diodes

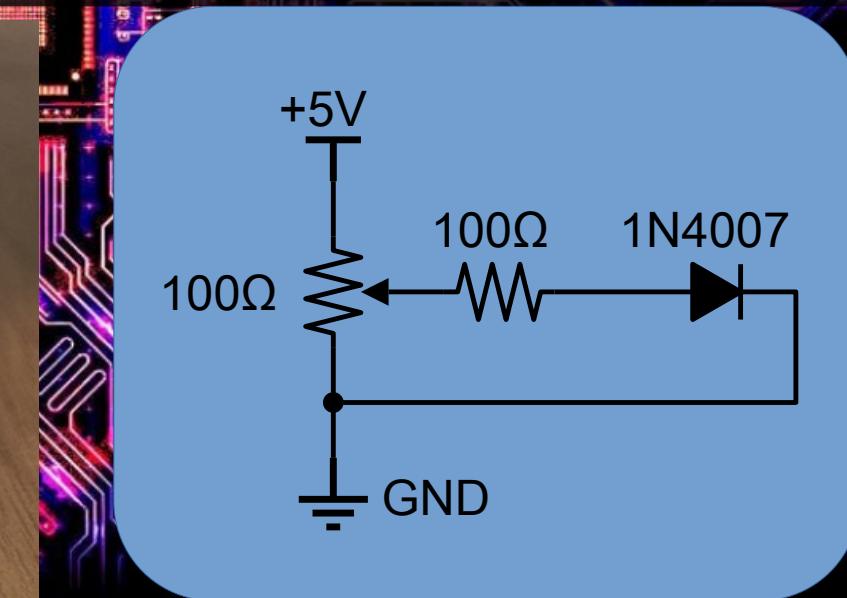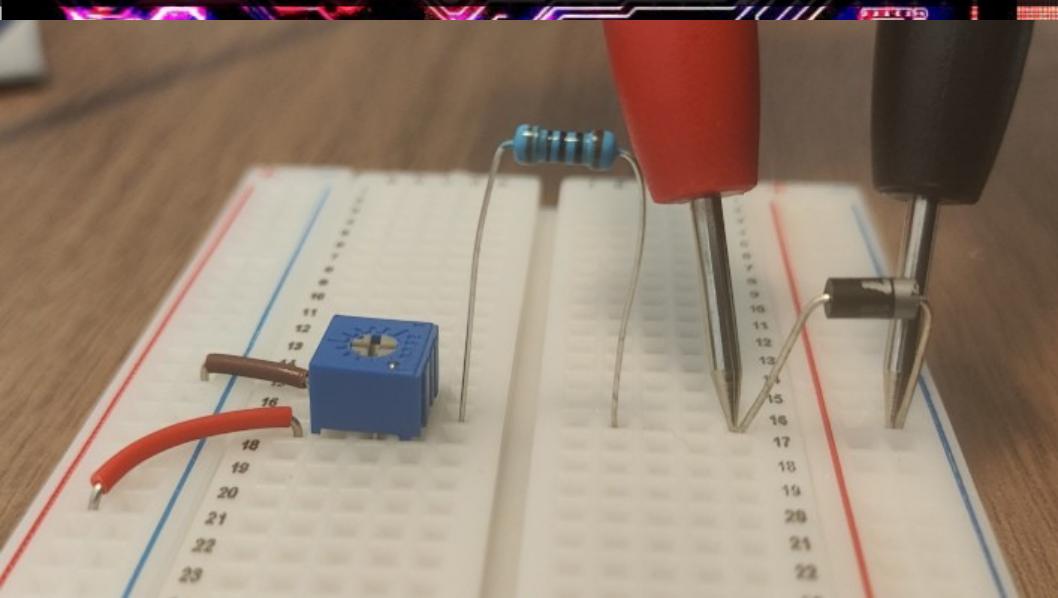- Learning objective completed:
 - Safely measure the **forward current** through a diode with changing **voltage** across the diode



Understanding Diodes

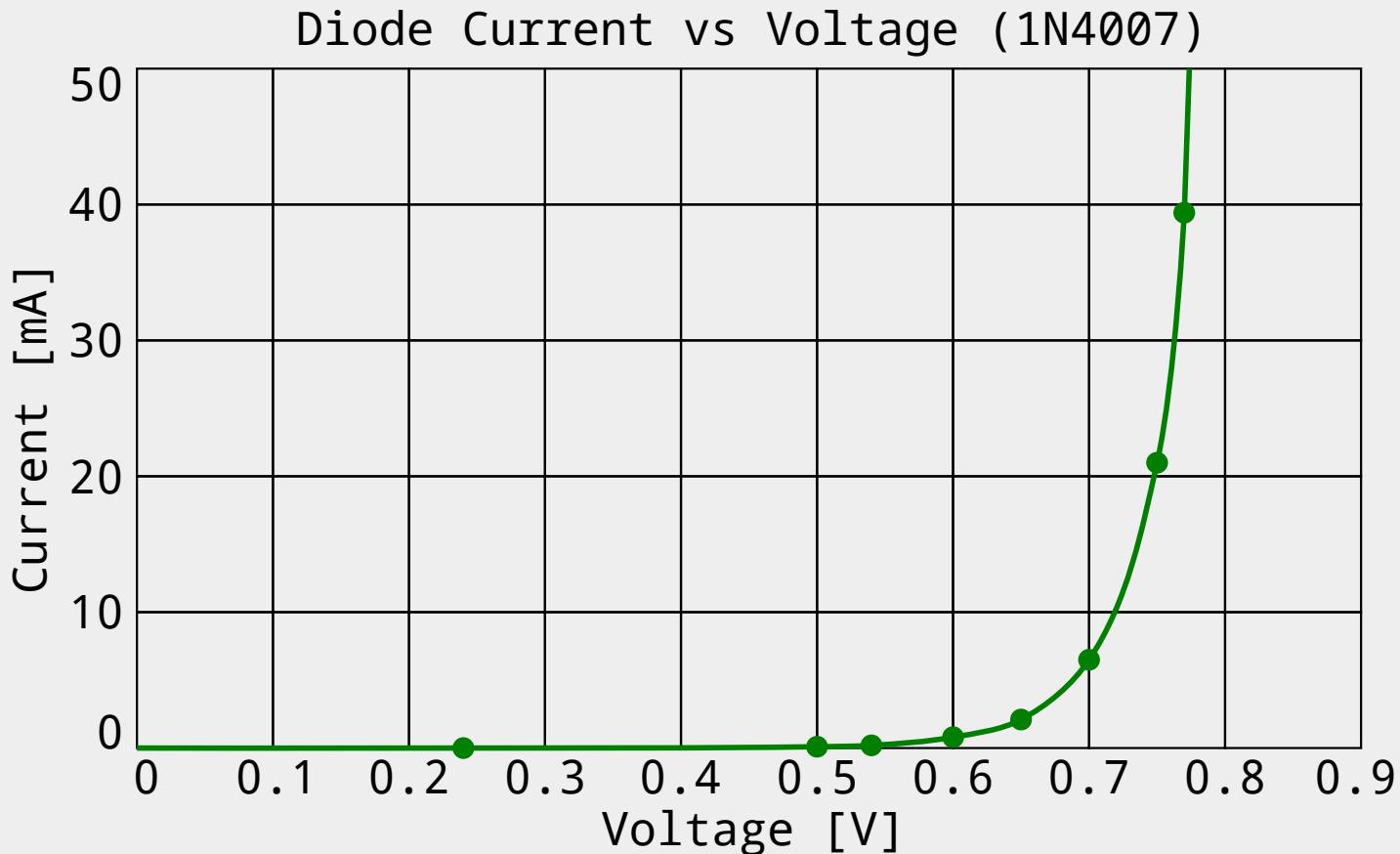

Unlike resistors,
diodes do not
follow Ohm's Law



Understanding Diodes



- A **light emitting diode**, or LED, is a diode that also emits light

LEDs (light emitting diodes)




Understanding Diodes

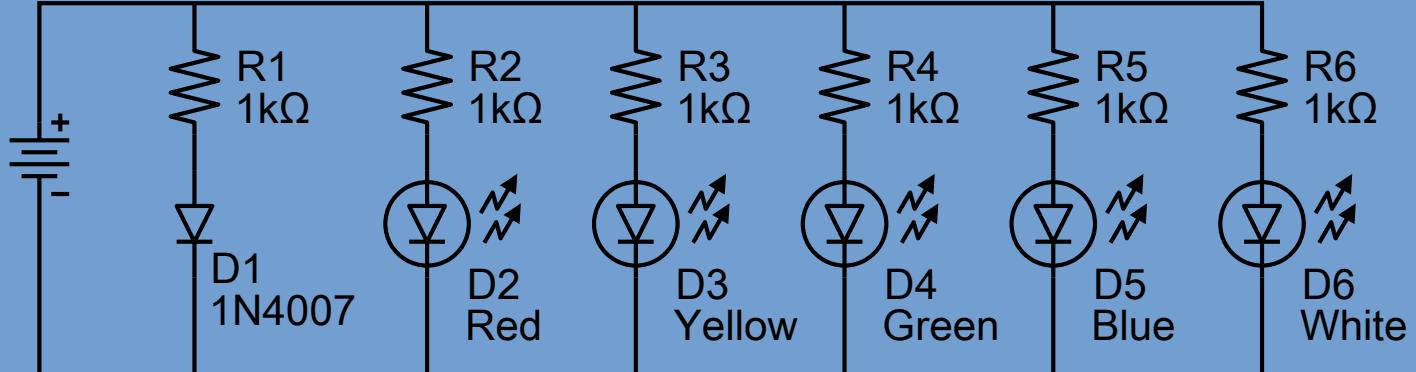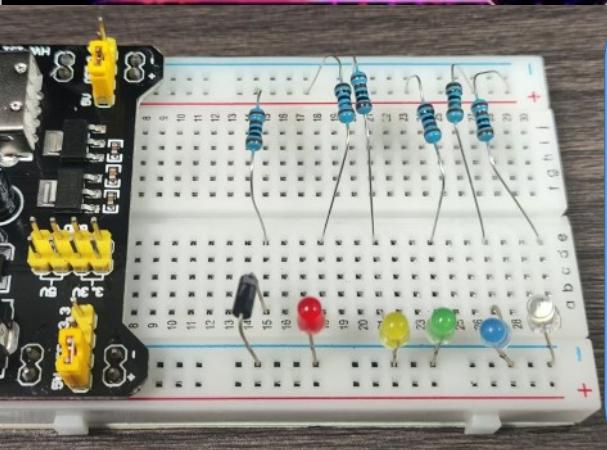
- Learning objective completed:
 - Safely measure and understand how the **color** of an LED affects the **voltage drop** across the LED





Electronic Engineering Club

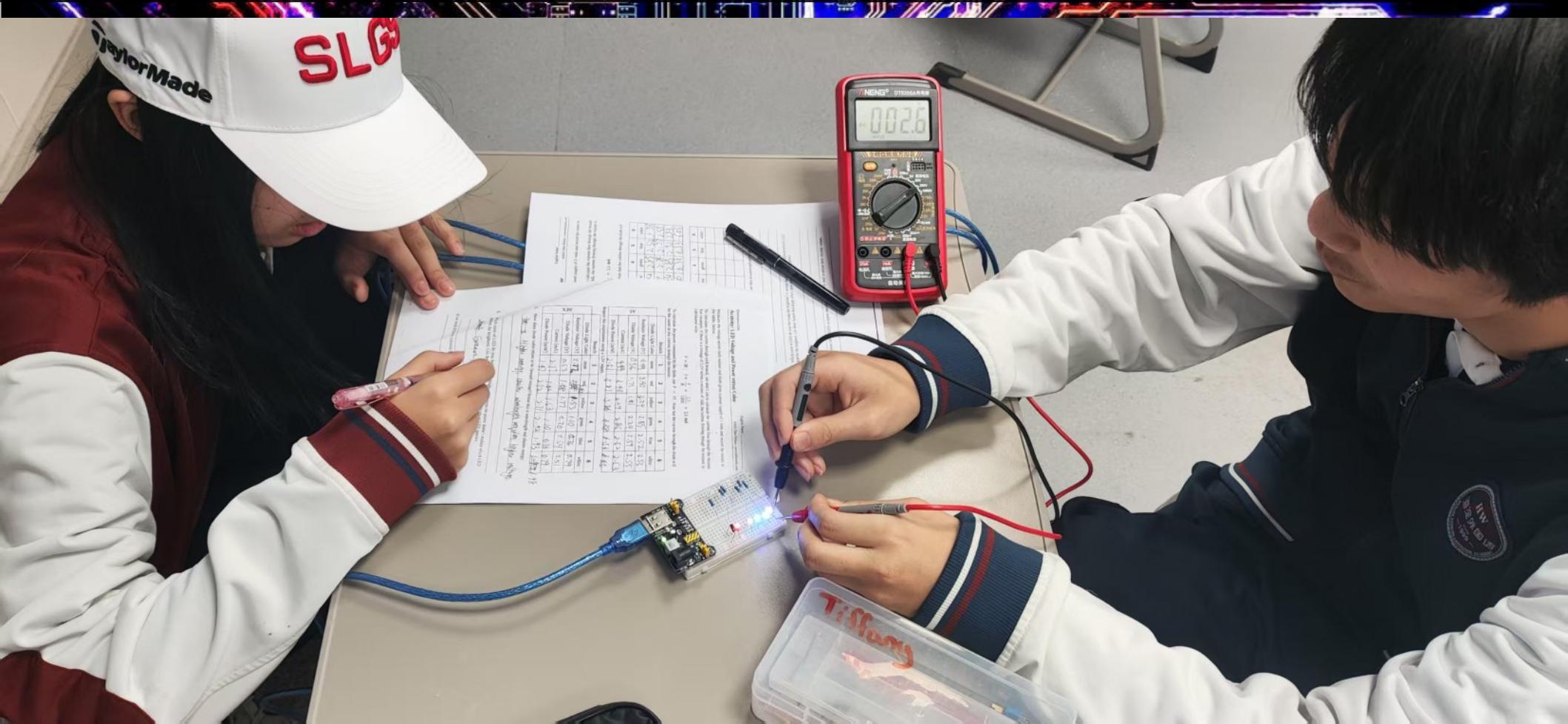



Understanding Diodes

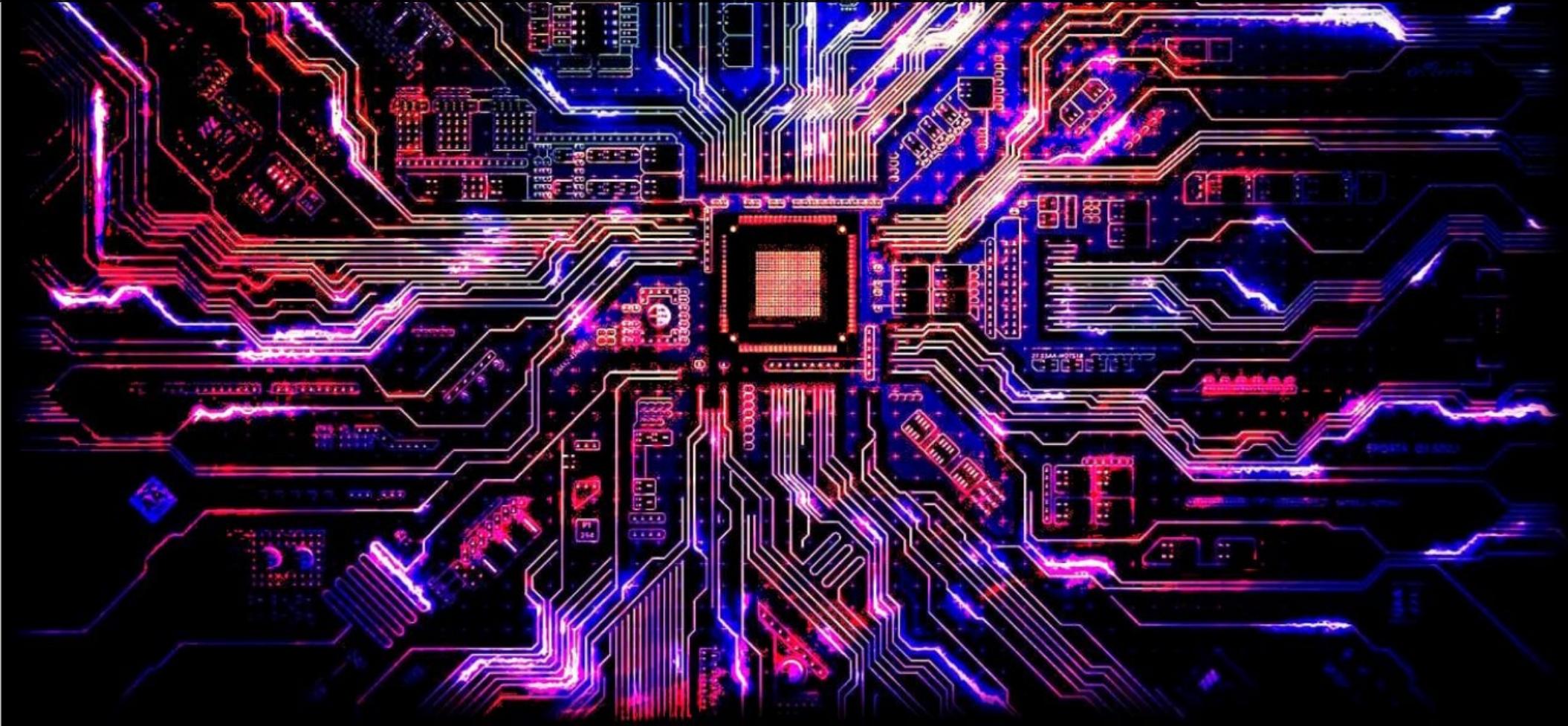

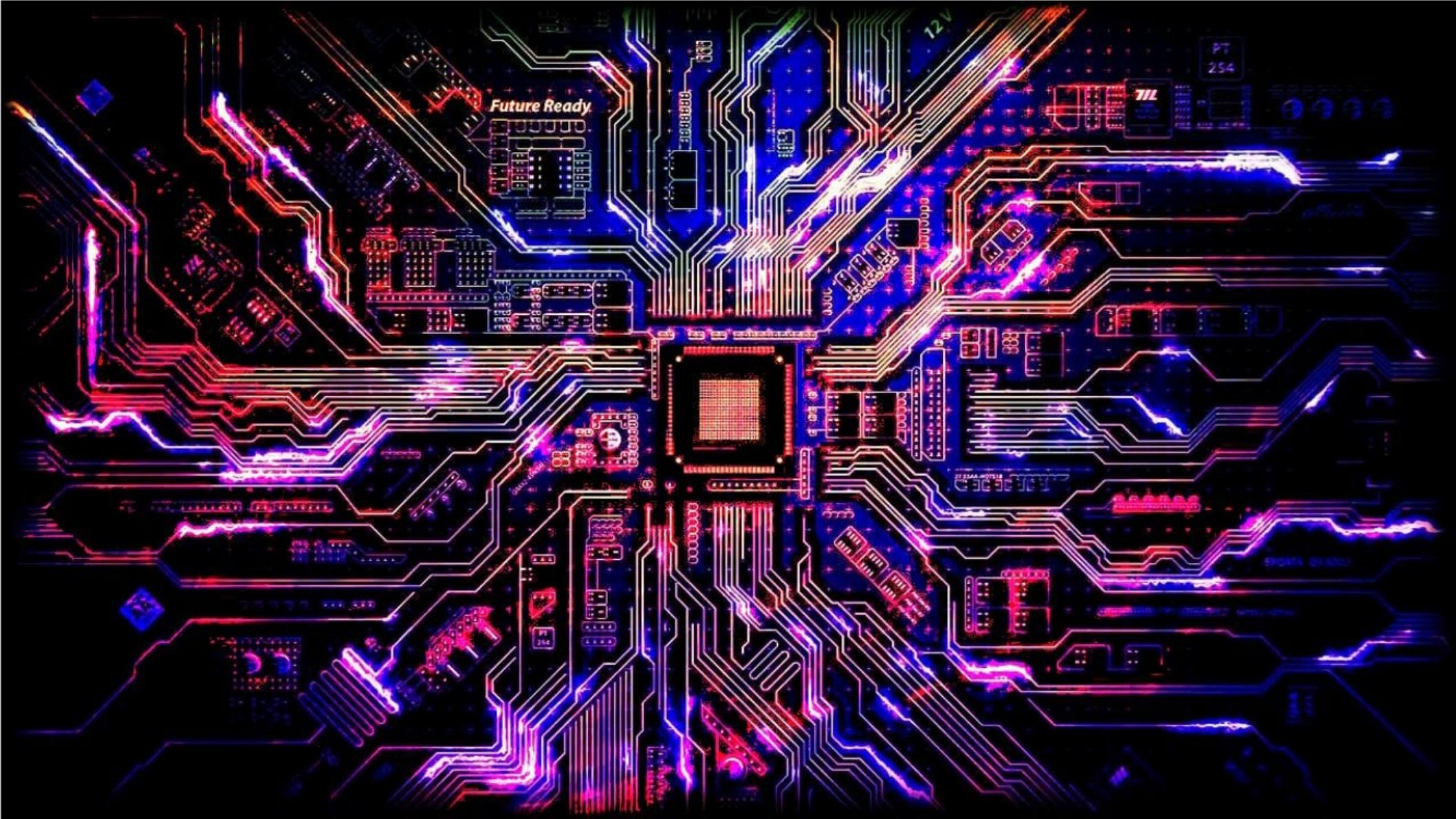

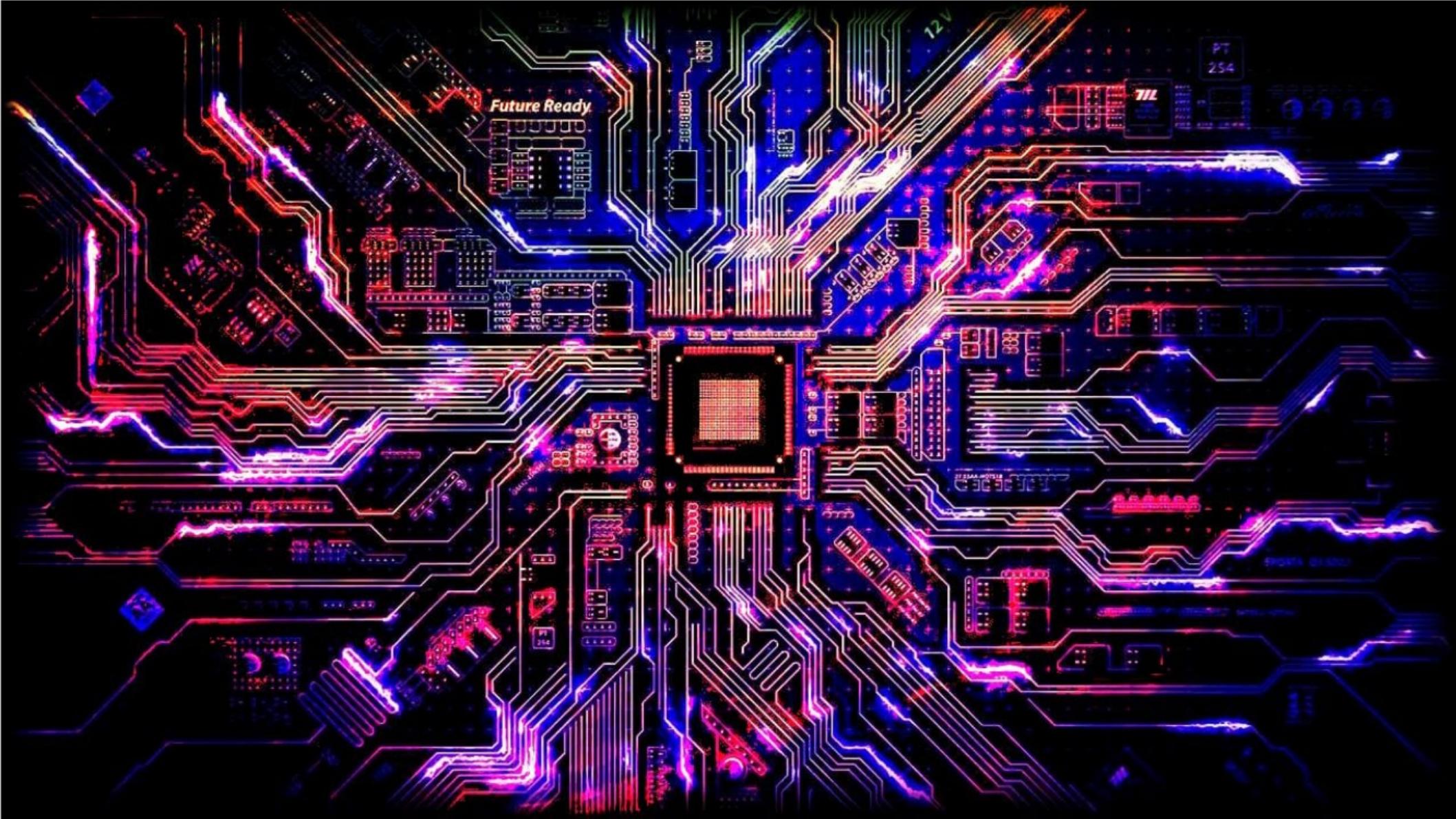

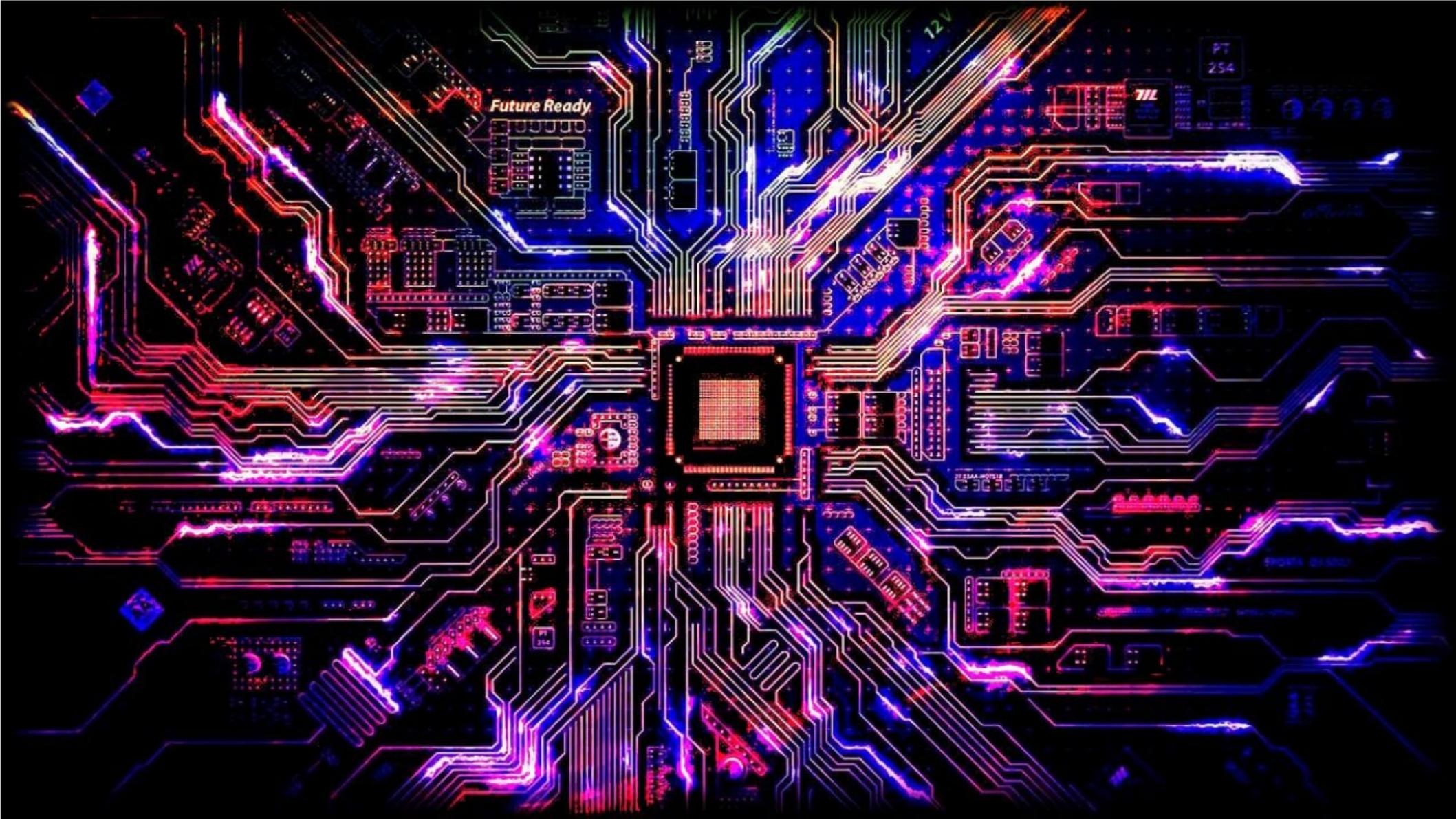

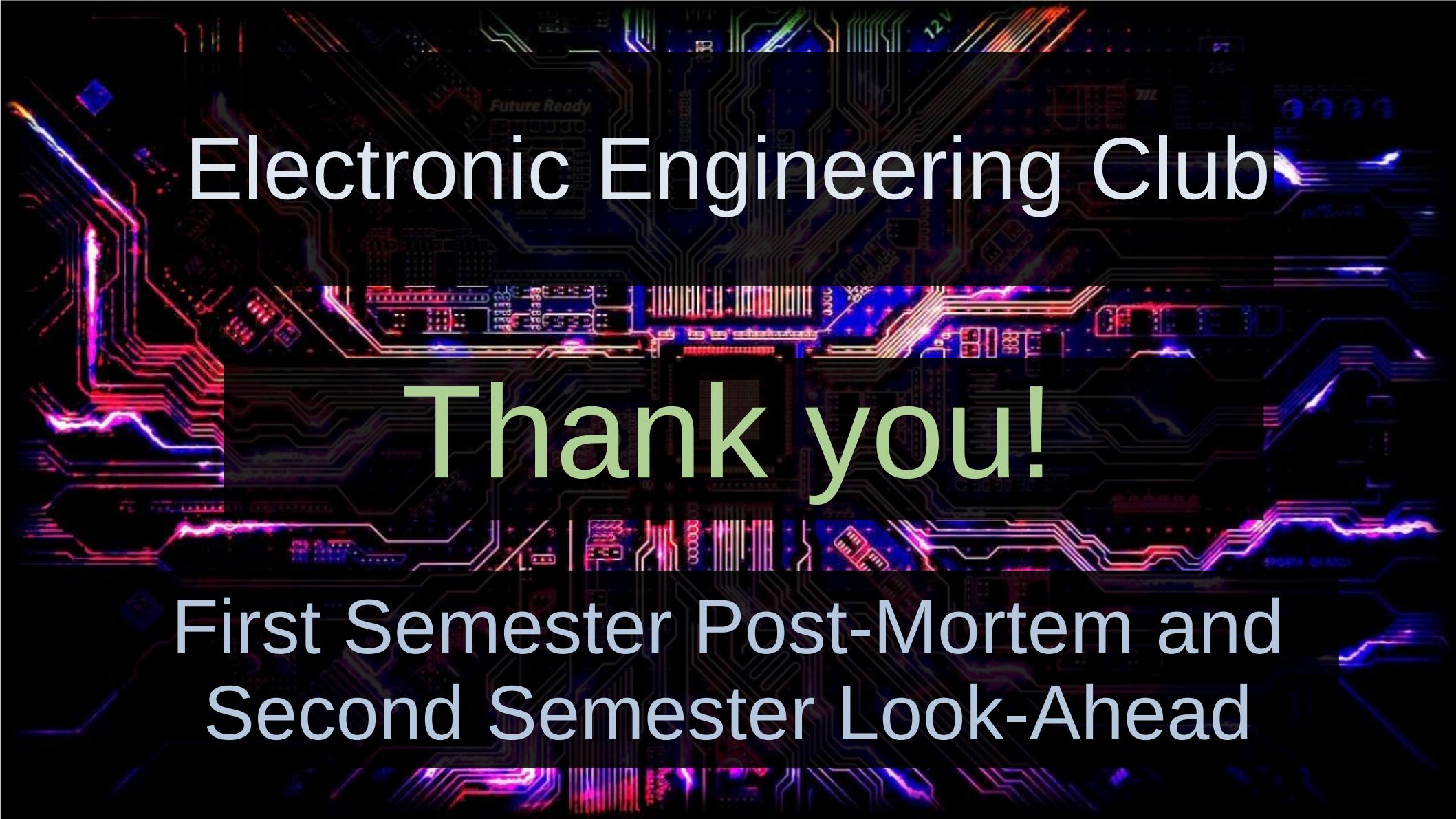

Electronic Engineering Club

Thank you!

First Semester Post-Mortem and
Second Semester Look-Ahead