

Basic Electronics

Electronics



Resistance Practice

Lecture Contents

- Kirchhoff's Current and Voltage Laws
- Resistance Practice Worksheet – Question 2
 - Photos to aid in understanding of the question

Kirchhoff's Current Law

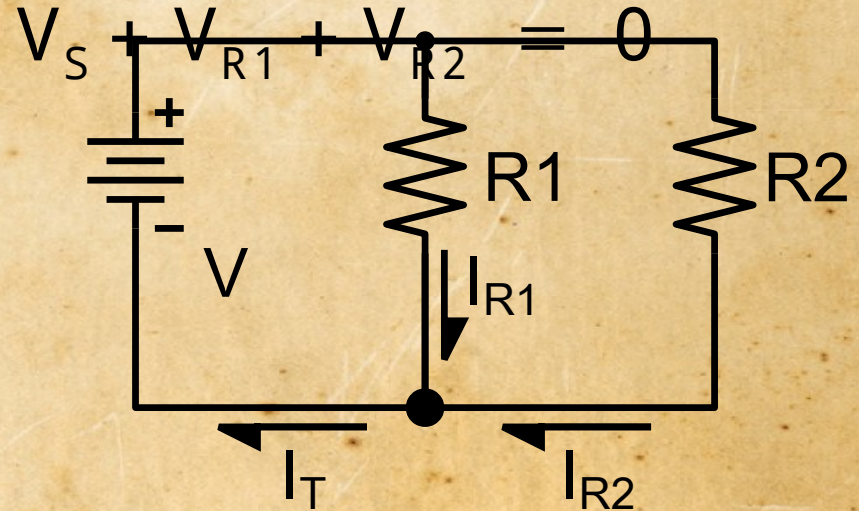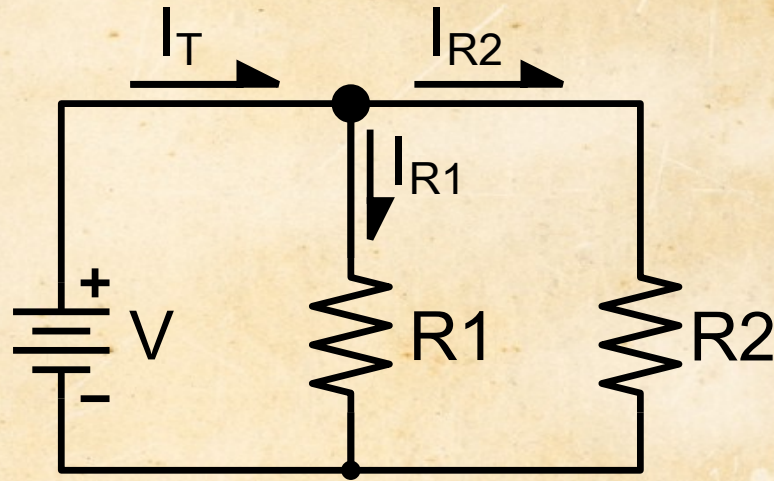
- the sum of all currents into a node equals the sum of all currents out of the node.*



$$I_T = I_{R1} + I_{R2}$$

Kirchhoff's Voltage Law

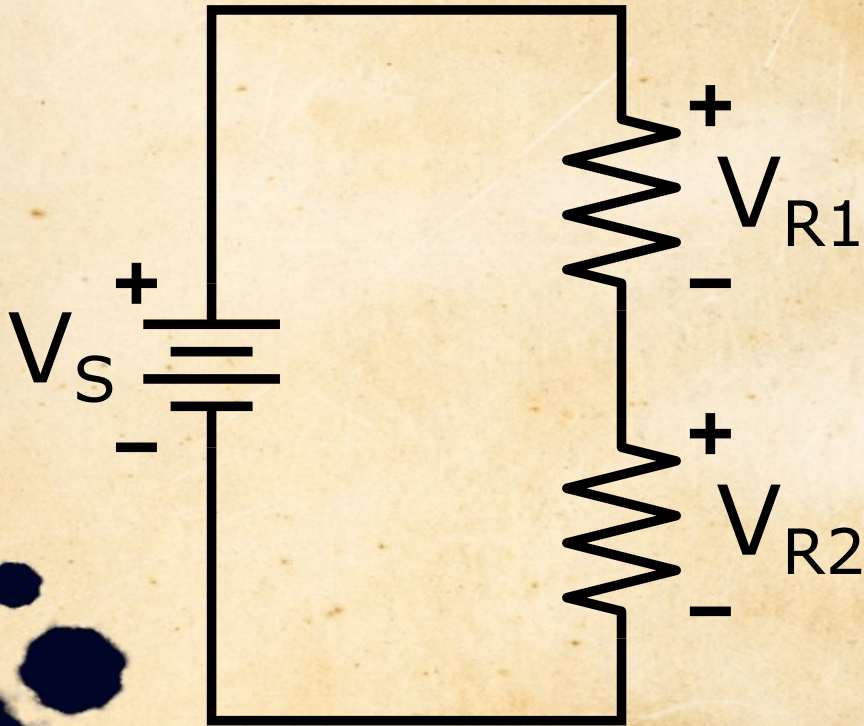- the algebraic sum of all voltages around any closed loop is zero.*



$$V_S + (-V_{R1}) + (-V_{R2}) = 0$$

$$V_S = V_{R1} + V_{R2}$$


Question 2a

- Ohmmeter set to 20M Ω
- Press a finger of one hand to one lead
- Press a finger of the opposite hand to the other lead
- Record the resistance value




Question 2b

- Ohmmeter set to 20M Ω
- Press one lead of a 1M Ω resistor to the Ohmmeter lead using the finger of one hand
- Press the other lead of the 1M Ω resistor to the other Ohmmeter lead using the finger of the other hand
- Record the resistance value

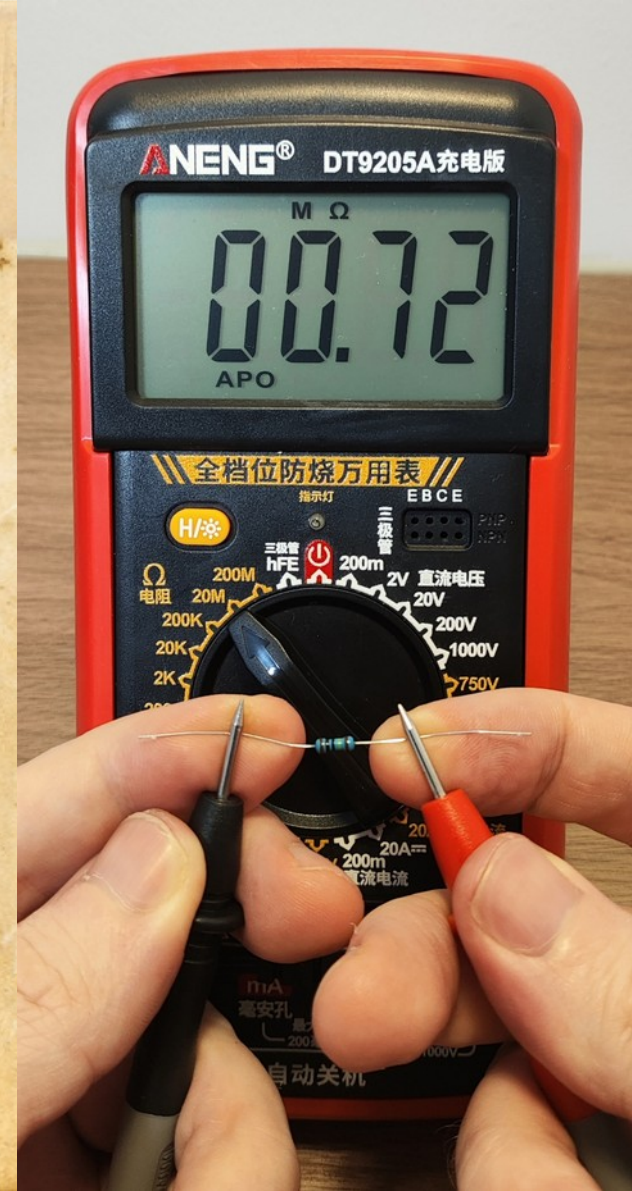

Question 2c

- Ohmmeter set to $20\text{M}\Omega$
- Measure the resistance of the resistor without contact to skin or any other circuit.
- Record the resistance value

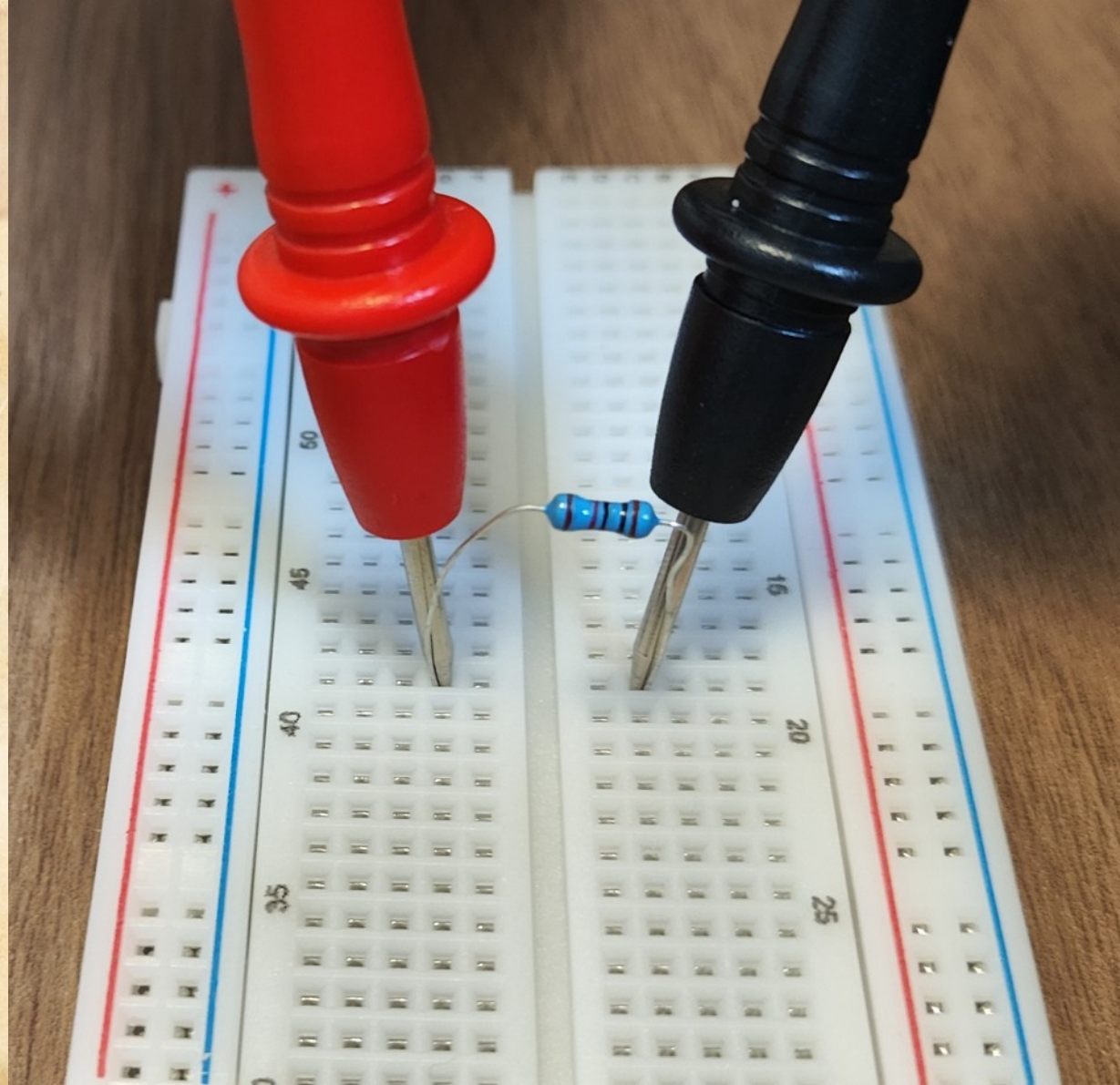

Question 2d

- Use one of these two formulas

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \dots$$

$$R_T = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

- to calculate the combined resistance of these in parallel:
 - your skin (measured in question 2a)
 - the resistor on it's own (measured in question 2c)
- Compare this result to the measurement you recorded for question 2b.

Question 2e

- Again use one of these two formulas

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \dots \qquad R_T = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

- to calculate the combined resistance of these in parallel:
 - your skin (measured in question 2a)
 - a 10kΩ resistor (not measured in our activity)
- Compare how much your skin resistance affects the measurement of:
 - a very large resistor value, such as 1MΩ
 - a lower resistor value, such as 10kΩ

Conclusion

- When accuracy is important, or when measuring very large resistor values, do not contact the resistor with your skin.
- For quick estimations, especially of lower resistor values, it is fine to hold the resistor in your hand during measurements.



Basic Electronics

Electronics

Resistance Practice