

# Electronics

Internal Resistance





# Lecture Contents

- Kirchhoff's Current and Voltage Laws
- Internal Resistance Worksheet
  - Photos to aid in understanding of the question


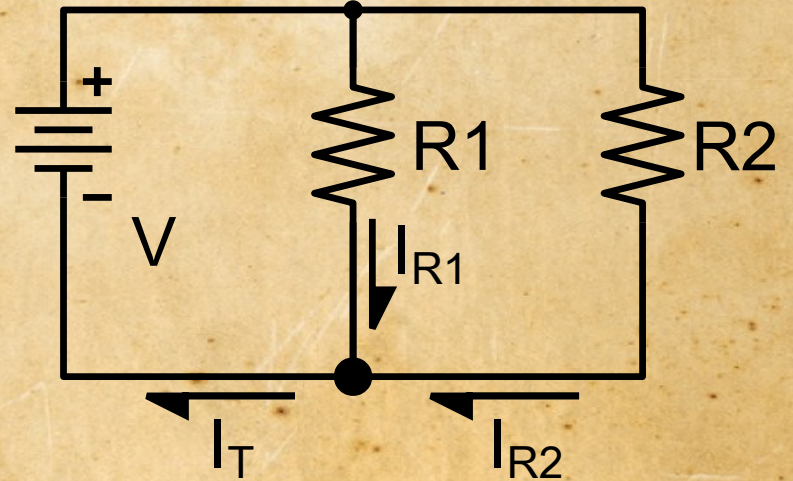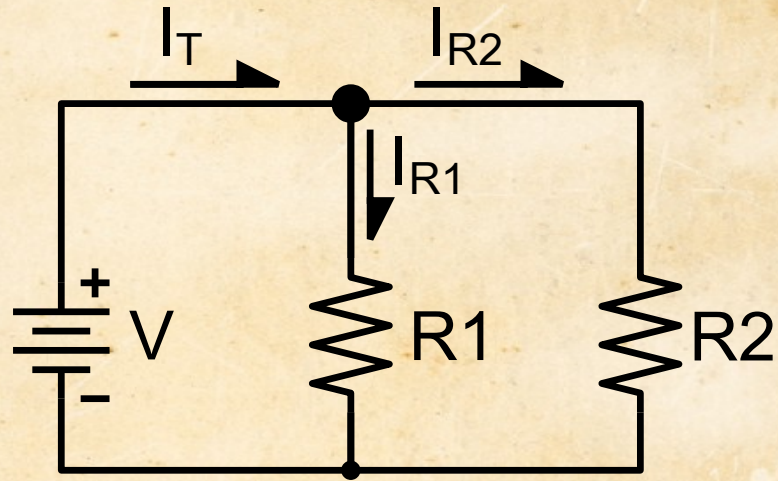
# Kirchhoff's Current Law (Q2)

- the sum of all currents into a node equals the sum of all currents out of the node.*




$$I_T = I_{R1} + I_{R2}$$


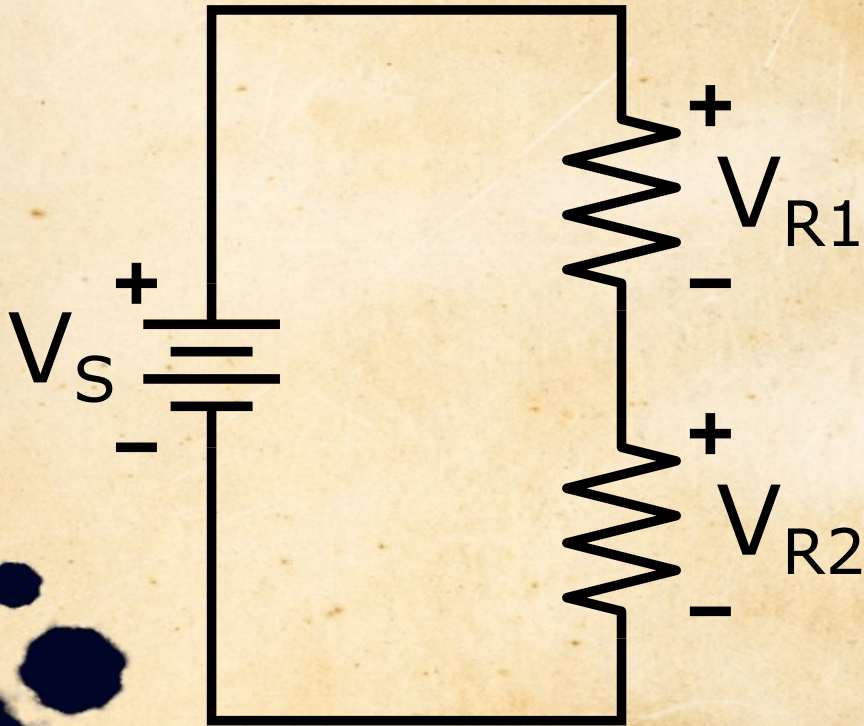
# Kirchhoff's Voltage Law (Q4)

- the algebraic sum of all voltages around any closed loop is zero.*



$$V_S + (-V_{R1}) + (-V_{R2}) = 0$$

$$V_S = V_{R1} + V_{R2}$$




# Equivalent Resistance (Q1a,1b)

- Series Resistance



$$R_T =$$

- Parallel Resistance

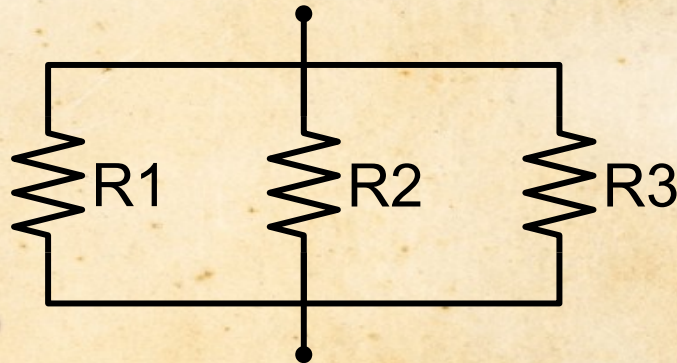

$$\frac{1}{R_T} =$$




# Equivalent Resistance (Q1a,1b)

- Series Resistance



$$R_T = R_1 + R_2 + R_3$$



- Parallel Resistance

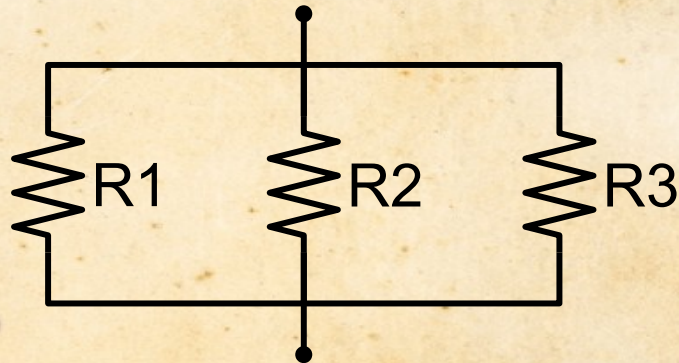

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



# Ohm's Law and Power (Q1c,1d)

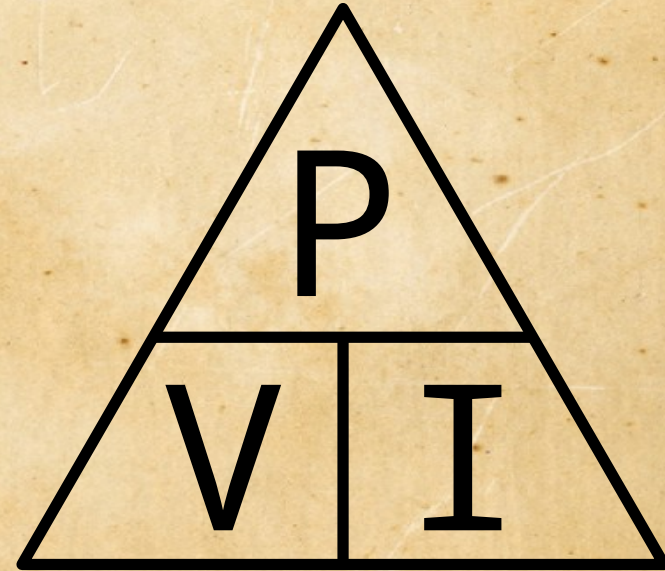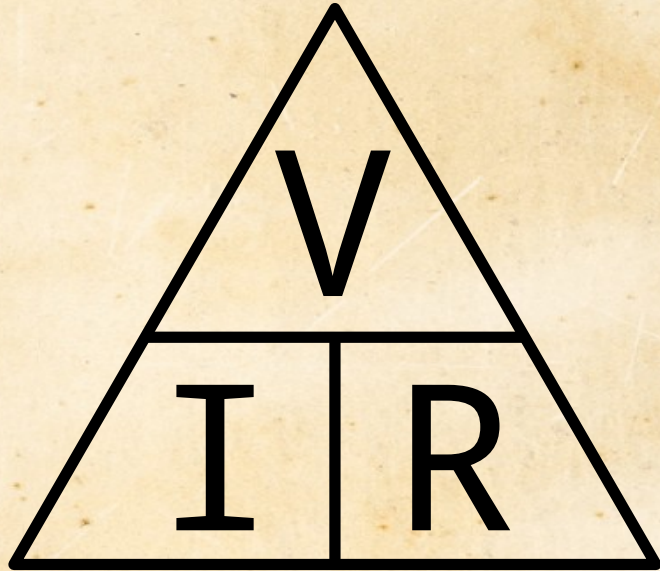



## Question 3a



- Calculate the total resistance for one, two, three, and four resistors, using the formula:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$


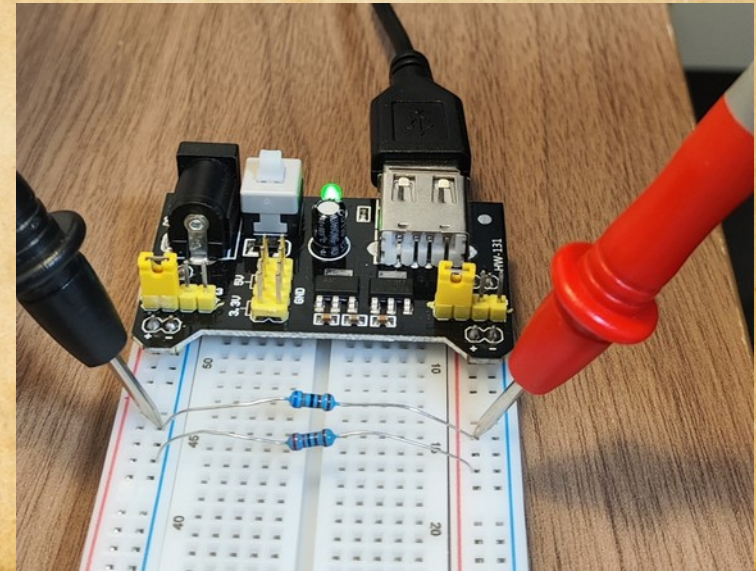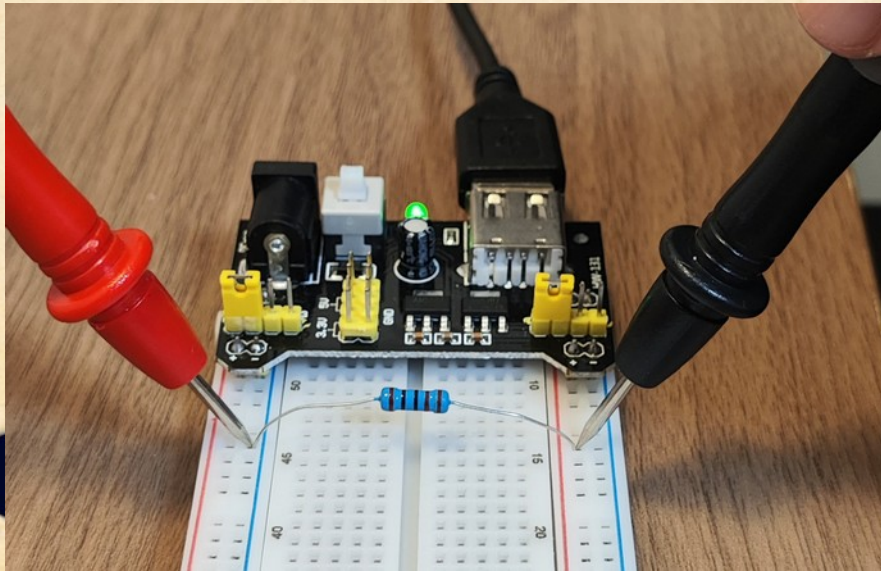
## Question 3b


- Ensure multimeter is on voltage setting → → → → →
- Measure the voltage across zero then one resistor, ...then two, then three, then four.





# Question 3b



- Using wires might make things easier

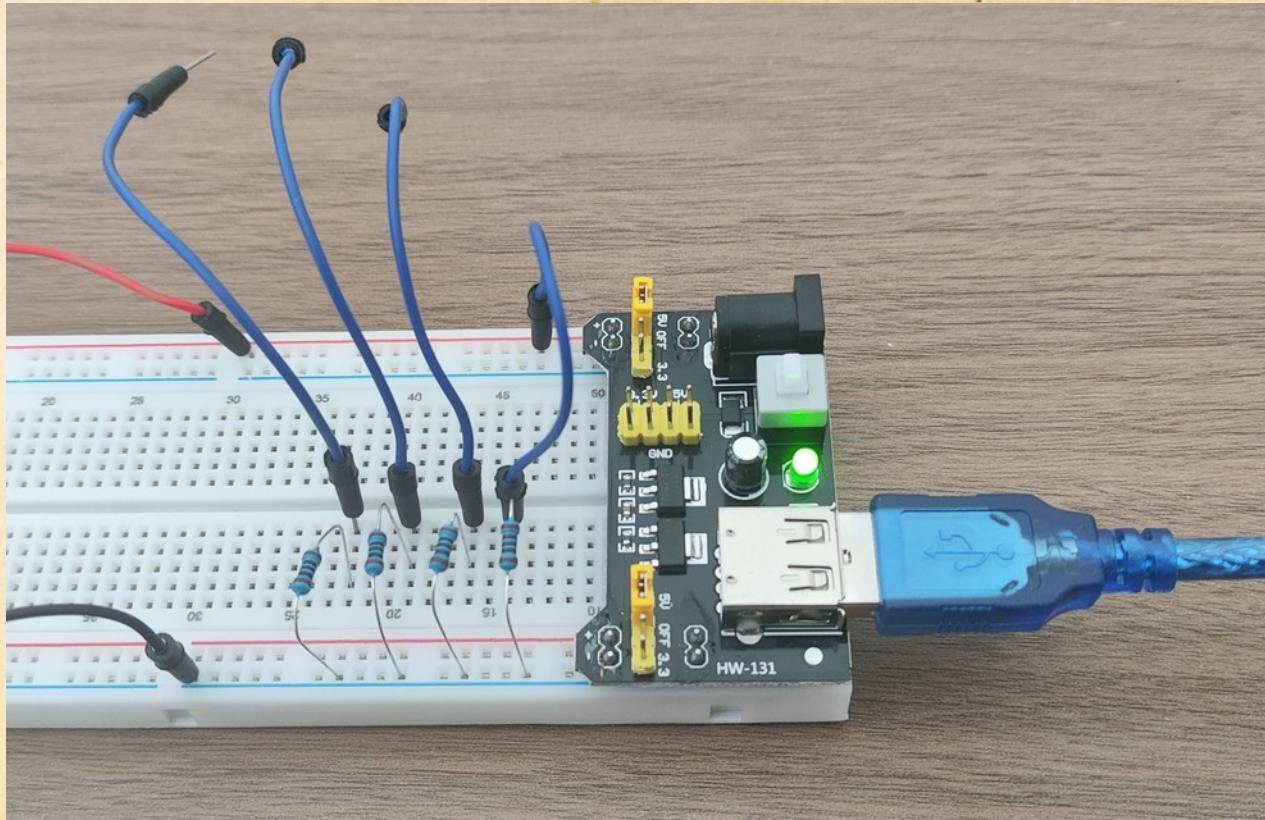


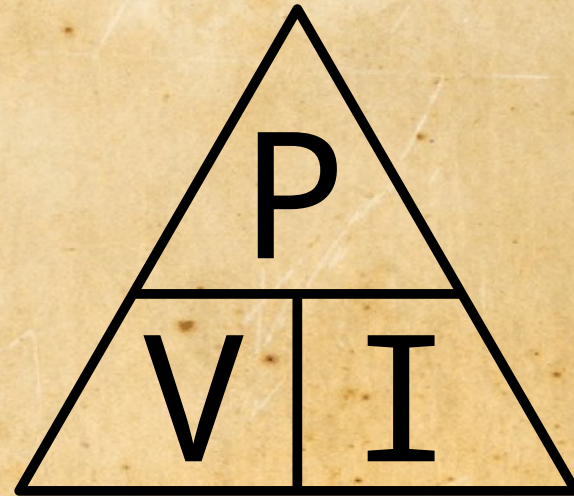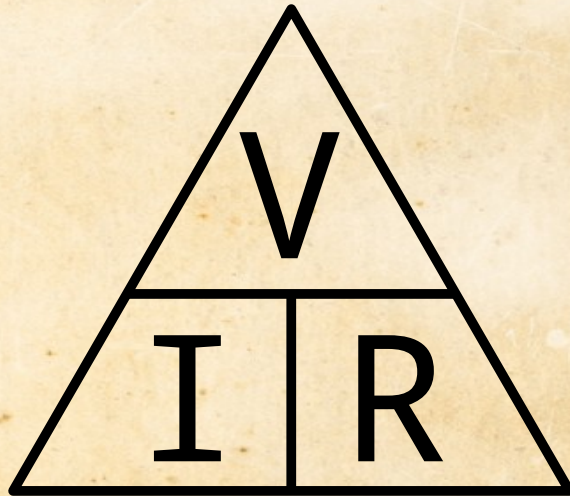
## Question 3c,d


- 3c) Calculate the total current for one, two, three, and four resistors, using Ohm's law
- 3d) Calculate the total power dissipated for one, two, three, and four resistors




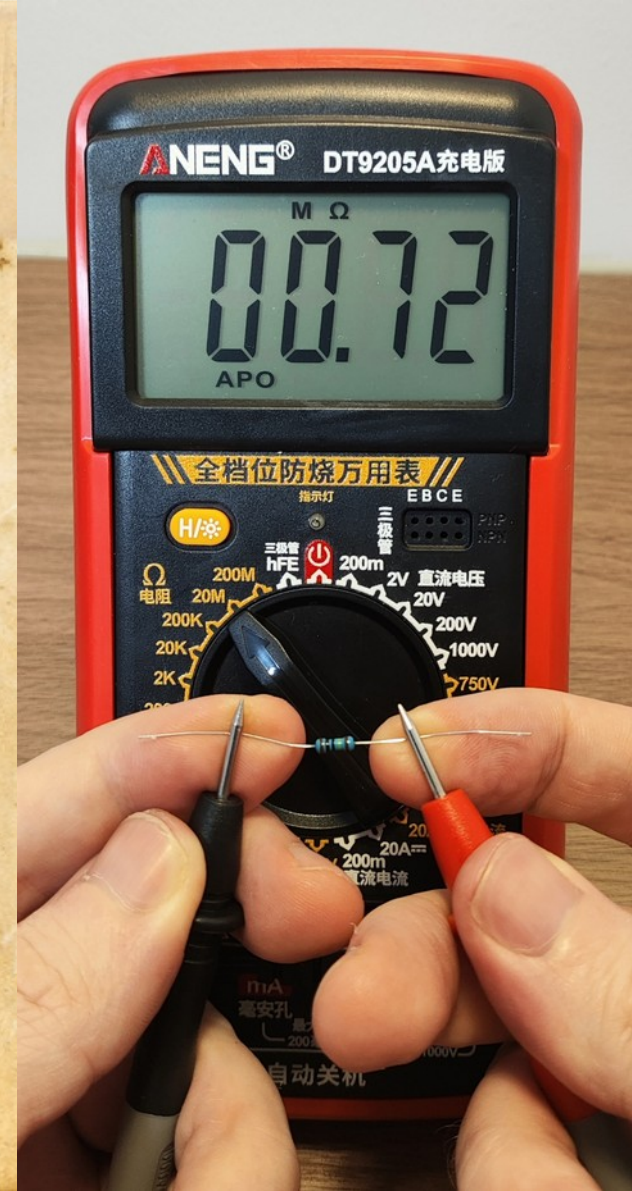
## Question 2b


- Ohmmeter set to 20M $\Omega$
- Press one lead of a 1M $\Omega$  resistor to the Ohmmeter lead using the finger of one hand
- Press the other lead of the 1M $\Omega$  resistor to the other Ohmmeter lead using the finger of the other hand
- Record the resistance value




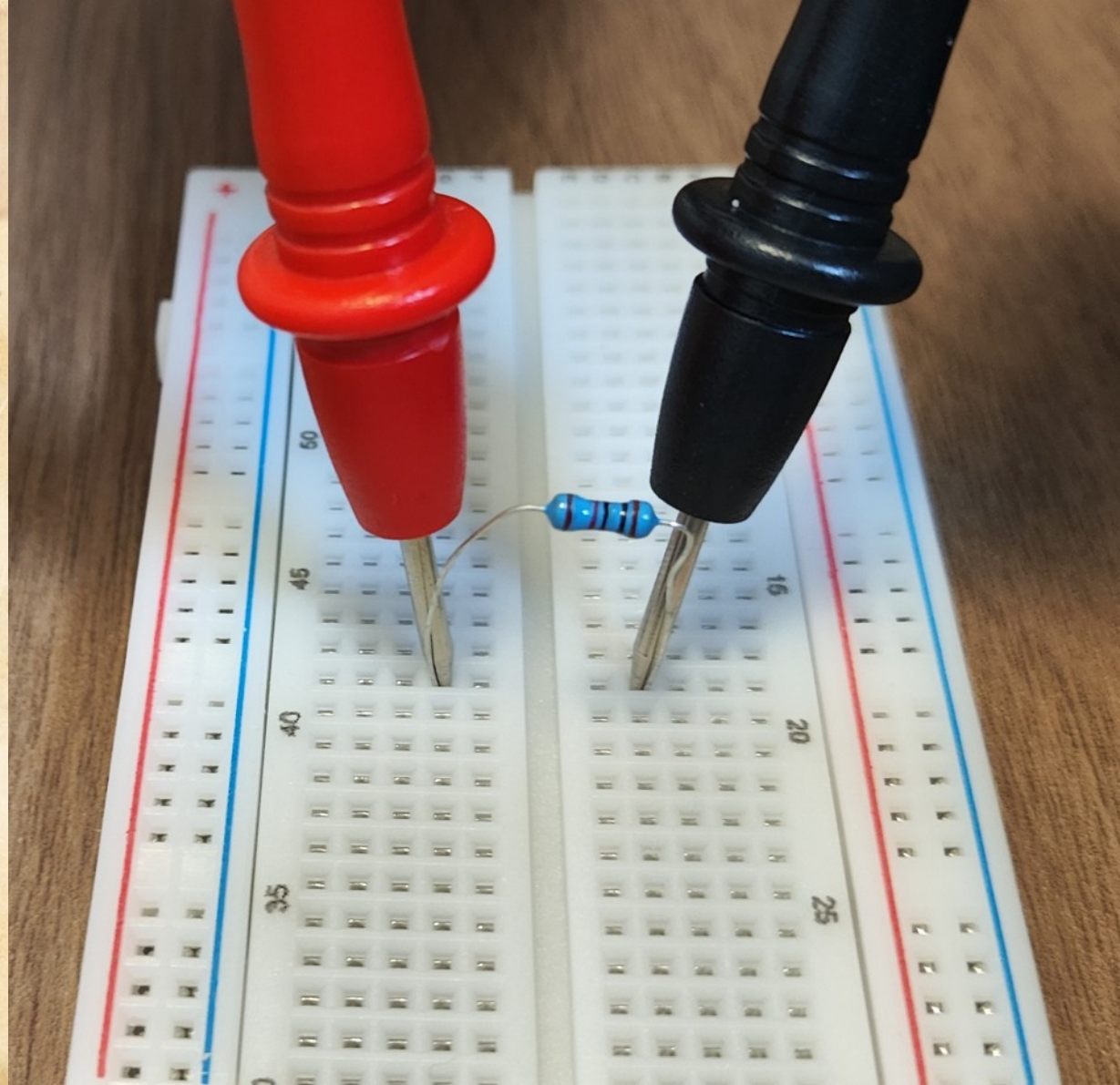
## Question 2c

- Ohmmeter set to  $20\text{M}\Omega$
- Measure the resistance of the resistor without contact to skin or any other circuit.
- Record the resistance value





## Question 2d

- Use one of these two formulas

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \dots \qquad R_T = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

- to calculate the combined resistance of these in parallel:
  - your skin (measured in question 2a)
  - the resistor on it's own (measured in question 2c)
- Compare this result to the measurement you recorded for question 2b.



## Question 2e

- Again use one of these two formulas

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \dots$$

$$R_T = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

- to calculate the combined resistance of these in parallel:
  - your skin (measured in question 2a)
  - a 10kΩ resistor (not measured in our activity)
- Compare how much your skin resistance affects the measurement of:
  - a very large resistor value, such as 1MΩ
  - a lower resistor value, such as 10kΩ



# Conclusion

- When accuracy is important, or when measuring very large resistor values, do not contact the resistor with your skin.
- For quick estimations, especially of lower resistor values, it is fine to hold the resistor in your hand during measurements.





## Question 5

- **ideal voltage** – the voltage you measured across the power supply when no resistors were connected
- **load resistance** – the calculated resistance for four parallel resistors
- **load voltage drop** – the measured voltage across four parallel resistors connected to the power supply
- **load current** – the calculated total current when four parallel resistors are connected (the current out of the power supply)
- **voltage across internal resistor** – calculated by:  
**ideal voltage – load voltage drop**



# Electronics

Internal Resistance