

Write the answer to Procedure 2 part 2 in the box below:  
Describe how the voltage changes when the capacitor circuit is opened (Open-circuit voltage).

time [s]	charging			discharging		
	measured capacitor voltage [V]	calculated resistor voltage [V]	calculated current [μA]	measured capacitor voltage [V]	calculated resistor voltage [V]	calculated current [μA]
0						
5						
10						
15						
20						
25						
30						
35						
40						
45						
50						
55						
60						
65						
70						
75						
80						
85						
90						

